

Total No. of Printed Pages—7

4 SEM TDC PHYH (CBCS) C 10

2024

(May/June)

PHYSICS

(Core)

Paper : C-10

(Analog Systems and Applications)

Full Marks : 53

Pass Marks : 21

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct option : 1×5=5

(a) The width of the depletion layer of a junction

(i) is independent of applied voltage

(ii) is increased under reverse bias

(iii) decreases with light doping

(iv) increases with heavy doping

(2)

- (b) The colour of the emitted light of LED depends on the
- (i) construction method
 - (ii) applied voltage
 - (iii) energy gap of the material used
 - (iv) None of the above
- (c) In RC coupled amplifier, voltage gain over mid-frequency range
- (i) is increasing
 - (ii) is constant
 - (iii) is decreasing
 - (iv) is zero
- (d) Oscillators employ
- (i) negative feedback
 - (ii) no feedback
 - (iii) positive feedback
 - (iv) None of the above

(3)

- (e) Open-loop voltage gain of OP-AMP
- (i) is small
 - (ii) is large
 - (iii) is zero
 - (iv) None of the above
2. (a) What happens to the depletion region of junction diode under forward and reverse bias condition? Explain. 3
- Or
- Define Fermi level in a semiconductor. How does its position change when (i) donor and (ii) acceptor are added to the semiconductor? 1+1+1=3
- (b) Derive an expression for the width of depletion layer of a $p-n$ junction diode. 4
- Or
- Define the mobility of charge carriers and conductivity. What is the effect of temperature on the conductivity of a semiconductor?

(4)

3. (a) Explain with circuit diagram the action of Zener diode as a voltage regulator. 3
- (b) Write about working and construction of photovoltaic cell. 2

4. (a) What do you mean by quiescent point or Q-point? What is the best position of Q-point on the DC load line in the transistor characteristics? 2
- (b) Explain active region, saturation region and cut-off region in transistor operation. 3

Or

The collector leakage current in a transistor is $300 \mu\text{A}$ in CE arrangement. If the transistor is now connected in the CB arrangement, what will be the leakage current? Given $\beta = 100$.

5. (a) Draw a circuit for voltage-divider bias method. What are its advantages and disadvantages? 1+2=3
- (b) Derive expression for the current gain and the voltage gain of a single-stage common-emitter transistor amplifier using h -parameters. 3

(5)

- (c) A CE transistor amplifier is connected with a load resistance $2 \text{ k}\Omega$. If the h -parameters of the transistor are $h_{ie} = 1000 \Omega$, $h_{re} = 10^{-4}$, $h_{fe} = 100$ and $h_{oe} = 12 \times 10^{-6} \text{ S}$, find the current gain, input impedance and voltage gain. 2

6. (a) Draw the circuit diagram of an RC coupled transistor amplifier and give its mid-frequency equivalent circuit. Derive an expression for gain at the mid-frequency range. 2+2=4

- (b) What is non-linear distortion? How can it be minimized? 1+2=3

- (c) Calculate the Barkhausen's criterion for self-sustained oscillations. 3

Or

An RC phase-shift oscillator has the parameter values $R_L = 3.3 \text{ k}\Omega$, $R = 5.6 \text{ k}\Omega$ and $C = 0.01 \mu\text{F}$. Calculate frequency of oscillations and the h_{fe} required for sustaining the oscillations.

(6)

7. (a) Draw the basic non-inverting amplifier with an input resistance R_1 and a feedback resistance R_f . Assuming the OP-AMP to be ideal, derive the expression for the voltage gain of the non-inverting amplifier. 1+3=4

Or

Calculate the CMRR of OP-AMP. 4

- (b) Explain with circuit diagram of an OP-AMP as integrator. 3

Or

The input to the differentiator OP-AMP is a sinusoidal voltage of peak value 10 mV and frequency 2 kHz. Find the output, if $R = 200 \text{ k}\Omega$ and $C = 2 \mu\text{F}$.

- (c) Explain the significance of virtual ground of a basic inverting amplifier. What do you understand by closed-loop and open-loop voltage gain of an OP-AMP? 3

Or

Consider the inverting OP-AMP with $R_1 = 10 \text{ k}\Omega$, $R_f = 100 \text{ k}\Omega$, $V_{in} = 1 V_{pp}$ and power supply voltages $\pm 18 \text{ V}$. Find (i) closed-loop voltage gain and (ii) the maximum operating frequency. The slew rate is $0.5 \text{ V}/\mu\text{s}$.

(7)

8. Explain the working of a binary weighted-resistor network. 3

Or

Briefly describe the resolution (step size) and accuracy specifications of a D/A converter.
