

Total No. of Printed Pages—4

3 SEM TDC PHYH (CBCS) C 7

2 0 2 4

(Nov/Dec)

PHYSICS

(Core)

Paper : C-7

(Digital Systems and Applications)

Full Marks : 53

Pass Marks : 21

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct answer : 1×5=5

(a) For observing a signal in an oscilloscope, it is to be applied

- (i) across its X-plates
- (ii) across its Y-plates
- (iii) to the horizontal amplifier
- (iv) to the trigger circuit

(b) The expression $\overline{ABC}$ can be simplified to

- (i) $\overline{A} \cdot \overline{B} \cdot \overline{C}$
- (ii) $AB + BC + CA$
- (iii) $AB + \overline{C}$
- (iv) $\overline{A} + \overline{B} + \overline{C}$

(2)

- (c) An X-OR gate produces high output only when its two inputs are
- (i) high
 - (ii) low
 - (iii) different
 - (iv) same
- (d) The half adder is constructed from
- (i) two X-OR gates
 - (ii) one X-OR gate and one OR gate with their inputs connected in parallel
 - (iii) one X-OR gate and one AND gate with their inputs connected in parallel
 - (iv) one X-OR gate and one NAND gate
- (e) If an inverter is placed at the input of an S-R flip-flop, the result is
- (i) D flip-flop
 - (ii) J-K flip-flop
 - (iii) T flip-flop
 - (iv) BCD decade counter

2. What is integrated circuit? How can a transistor be fabricated in an IC? 3

Or

Deduce an expression for deflection sensitivity of CRT.

(3)

3. (a) Convert hexadecimal number 4DFA into binary number. 2
- (b) Describe how NOR gate can be constructed using diodes and transistors. Explain their action with their truth table. 3
4. (a) State and prove De Morgan's two theorems. 3
- (b) Show that $AB + A\bar{B}C + B\bar{C} = AC + B\bar{C}$ using Boolean algebra. 3

Or

Simplify the expression

$$Y = ABCD + ABC\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}\bar{D}$$

using Karnaugh map and draw the logic circuit for the reduced expression. 3

5. Draw the logic diagram of multiplexer and explain it. 3

6. (a) Explain the circuit diagram of a full adder with truth table. 4

Or

What is the difference between adder and subtractor? Explain the circuit diagram of a half-subtractor. 1+3=4

- (b) Draw the logic diagram of 4-bit parallel-in parallel-out shift register. 2

7. What is flip-flop? Explain the operation of J-K flip-flop. 1+3=4
8. (a) Explain the operation of astable multivibrator using IC-555. 3
- Or
- Draw and explain the functional diagram of IC-555.
- (b) What is the difference between decade counter and synchronous counter? 2
9. Write a short note on asynchronous counter. 4
10. (a) Write a short note on Random Access Memory (RAM). 2
- (b) Define primary and secondary memories. 2
11. (a) Explain with necessary diagram, the function of different pins of 8085 microprocessor. 5
- (b) Draw and explain the timing diagram for instruction MVI reg, data. 3

★ ★ ★