

3 SEM TDC PHYH (CBCS) C 7

2 0 2 0

(Held in April–May, 2021)

PHYSICS

(Core)

Paper : C-7

(**Digital Systems and Applications**)

Full Marks : 53

Pass Marks : 21

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct answer from the following : 1×5=5

(a) The signal to be observed on the screen of an oscilloscope is applied

- (i) across its X-plates
- (ii) across its Y-plates
- (iii) to the horizontal amplifier
- (iv) to the trigger circuit

(b) After counting 0, 1, 10, 11, the next binary number is

- (i) 12
- (ii) 100
- (iii) 101
- (iv) 110

(c) An X-OR gate produces an output only when its two inputs are

- (i) high
- (ii) low
- (iii) different
- (iv) same

(d) The expression \overline{ABC} can be simplified to

- (i) $\overline{A} \cdot \overline{B} \cdot \overline{C}$
- (ii) $AB + BC + CA$
- (iii) $AB + \overline{C}$
- (iv) $\overline{A} + \overline{B} + \overline{C}$

(e) If an inverter is placed at the input to an S-R flip-flop, the result is

- (i) D flip-flop
- (ii) J-K flip-flop
- (iii) T flip-flop
- (iv) BCD decade counter

(3)

2. Define deflection sensitivity of a CRT. Obtain an expression for the deflection sensitivity of the electrostatic type. 1+3=4
3. What is monolithic IC? Explain the steps involved in fabricating a diode in an IC. 3
4. (a) Convert the binary number 100111010·101010 into octal number. 2
(b) Describe how NOR gate can be constructed using diodes and transistors. Explain their action with their truth table. 3
5. (a) State and prove De Morgan's two theorems. 3
(b) Show that $AB + A\bar{B}C + B\bar{C} = AC + B\bar{C}$ using Boolean algebra. 3
- Or*
- Simplify the expression
$$Y = ABCD + ABC\bar{D} + A\bar{B}CD + A\bar{B}C\bar{D}$$
using Karnaugh map and draw the logic circuit for the reduced expression.
6. Draw the logic diagram of multiplexer and explain it. 3
7. (a) State the rules for binary subtraction. Explain 1's complement and 2's complement method with examples. 3

(4)

Or

- Draw the logic circuit diagram of a full subtractor. Find out its outputs and draw the truth table.
- (b) Draw the logic diagram of a half-adder and write its truth table. 2
8. What is flip-flop? Draw the logic diagram of J-K flip-flop and explain it. 1+3=4
9. (a) Draw and explain the functional diagram of IC-555. 3
- Or*
- With a circuit diagram, explain the operation of astable multivibrator using IC-555.
- (b) Draw the logic diagram of 4-bit serial-in, serial-out shift register. 2
10. Write a short note on asynchronous counter. 4
11. (a) Write a short note on Random Access Memory (RAM). 2
(b) Explain the function of ALU in microprocessor. 3
12. What is stack? What is the function of stack pointer? Discuss PUSH and POP operation. 4
- Or*
- Draw and explain the timing diagram for the instruction MVIR data.

★★★