

4 SEM TDC PHYH (CBCS) C 10

2023

(May/June)

PHYSICS

(Core)

Paper : C-10

(**Analog Systems and Applications**)

Full Marks : 53

Pass Marks : 21

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct answer : 1×5=5

(a) Under forward bias, current in a $p-n$ diode does not flow before it attains _____ in silicon and germanium $p-n$ junction diode respectively.

(i) 0.5 V and 0.7 V

(ii) 0.7 V and 0.3 V

(iii) 1.1 V and 0.7 V

(iv) 0.3 V and 0.7 V

(2)

(b) Avalanche breakdown is primarily dependent on the phenomenon of

- (i) doping
- (ii) ionisation
- (iii) recombination
- (iv) collision

(c) The value of α of a transistor is

- (i) more than 1
- (ii) less than 1
- (iii) 1
- (iv) 0

(d) In CE arrangement, the value of input impedance is approximately equal to

- (i) h_{ie}
- (ii) h_{oe}
- (iii) h_{re}
- (iv) None of the above

(3)

(e) Which of the following amplifiers cannot be used for audio frequency amplifier?

- (i) Class A
- (ii) Class B
- (iii) Class AB
- (iv) Class C

2. (a) Draw the energy band diagrams of n -type and p -type semiconductors indicating the position of Fermi level. 3

Or

Distinguish between static and dynamic resistance of a p - n junction diode. Do they depend on temperature and bias voltage? 2+1=3

(b) Explain the formation of barrier potential in a p - n junction. Derive an expression for the barrier potential of a p - n junction. 4

Or

Discuss different types of p - n junction diodes on the basis of method of fabrication.

(4)

3. (a) Draw the circuit diagram of a full-wave rectifier and calculate its ripple factor. 1+2=3
- (b) Write about the working and construction of a photodiode. 2
4. (a) What is a load line in the transistor characteristics? Explain its significance. 2
- (b) Explain with necessary diagram, the mechanism of current flows in an *n-p-n* transistor. 3

Or

A load resistance of $4\text{ k}\Omega$ is connected in collector circuit of a common emitter transistor amplifier with $V_{CC} = 12\text{ V}$. What are the cut-off point and saturation point of output characteristics of the amplifier? Find the coordinate of the operating point, if the zero signal base current is $20\text{ }\mu\text{A}$ and $\beta = 100$. 5

5. (a) Draw a fixed bias circuit. On the basis of stability factor, mention the merits and demerits of this circuit. 2+1=3

(5)

- (b) Starting from the two equations for the hybrid parameters, draw the *h*-parameter equivalent circuit for a common emitter transistor circuit. 3
- (c) In CE transistor amplifier, following current and voltages are found :
- (i) When output ac is short-circuited, $I_b = 20\text{ }\mu\text{A}$, $I_c = 2\text{ mA}$, $V_{be} = 20\text{ mV}$
- (ii) When input ac is open-circuited, $V_{bc} = 0.75\text{ mV}$, $I_c = 90\text{ }\mu\text{A}$, $V_{ce} = 1.5\text{ V}$
Find the *h*-parameters of the transistor. 2
6. (a) Explain the operation of a two-stage RC coupled CE transistor amplifier with a neat circuit diagram. 2+2=4
- (b) What is negative feedback? Explain with necessary frequency response curve, how the bandwidth of an RC coupled amplifier is modified when negative feedback is used. 1+2=3
- (c) Describe a Hartley or a Colpitts oscillator circuit and explain its operation. 3

(6)

7. (a) Draw the basic inverting amplifier with an input resistance R_1 and a feedback resistance R_f . Assuming the OP-AMP to be ideal, derive the expression for the voltage gain of the inverting amplifier.


2+2=4

- (b) Explain with circuit diagram of an OP-AMP as differentiator. 3

 - (c) Define CMRR and slew rate of an OP-AMP. What is the importance of CMRR? 2+1=3

Or

Determine the output voltage for the summing amplifier as shown below : 10



(7)

8. What is the function of a DAC? Write the advantage of the R-2R ladder type DAC over the weighted-resistor type DAC. 1+2=3

Or

Design a 4-bit weighted-resistor DAC whose full-scale output voltage is -5 V . The logic levels are $1 = +5\text{ V}$ and $0 = 0\text{ V}$. What is the output voltage, when the input is 1101? 3
